

# CS4125

## Design Pattern: A FIFO Module

黃稚存



國立清華大學  
資訊工程學系

Lecture 11

# An FSM Coding Practice for a FIFO Design

---

- Using the memory generator for simulation (and for synthesis later)
- A coding practice for an FSM
- Design target: FIFO
  - ◆ Start with spec and block diagram


# Specification

---

- Implement a FIFO design with 32 entries
  - ◆ Each has 8 bits
- The block diagram with its primary inputs and outputs
  - ◆ 8-bit data in
  - ◆ 8-bit data out
  - ◆ What else?

# Block Diagram

---

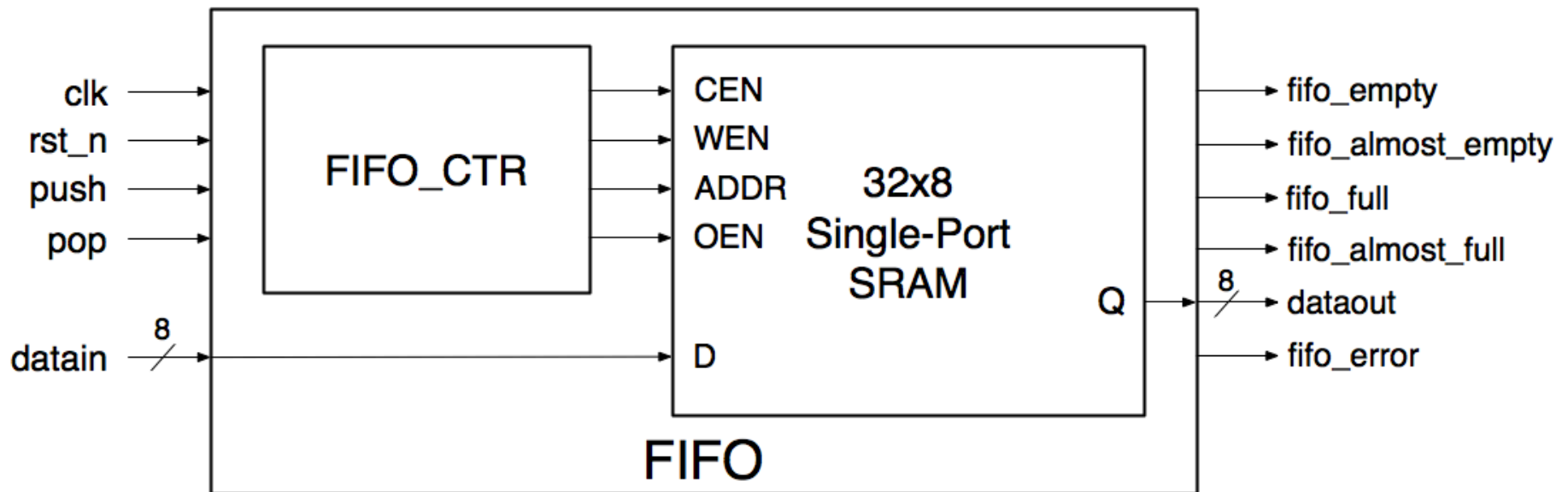

# Primary IOs and Block-Level Interconnection

---

- Inputs:
  - ◆ clk: clock
  - ◆ rst\_n: negative reset
  - ◆ push: a control signal to push a data
  - ◆ pop: a control signal to pop a data
  - ◆ datain: 8-bit input data
- Outputs:
  - ◆ dataout: 8-bit output data
  - ◆ fifo\_empty: a flag to indicate that the FIFO is empty
  - ◆ fifo\_almost\_empty:  
a flag to indicate the FIFO will be empty with one more pop
  - ◆ fifo\_full: a flag to indicate the FIFO is full
  - ◆ fifo\_almost\_full:  
a flag to indicate the FIFO will be full with one more push
  - ◆ fifo\_error: a flag to indicate error

# Primary IOs and Block-Level Interconnection


---

- Internal signals:
  - ◆ head, tail:

There are two pointers, head and tail, to indicate the beginning and end of the FIFO, respectively
  - ◆ Inputs to SRAM:
    - ▣ CEN, WEN, OEN, ADDR, D
  - ◆ Outputs from SRAM:
    - ▣ Q

# Two Pointers in FIFO

- head and tail are reset to zero

 

# FIFO Controller

## States and Input Control Signals

---

- FSM with 4 states
  - EMPTY, BETWEEN, FULL and READOUT
- Major operations of FIFO
  - Push
    - `RAM[head] = datain`
    - `head = (head + 1) % size_of_ram`
  - Pop
    - `dataout = RAM[tail]`
    - `tail = (tail + 1) % size_of_ram`
- Four possible input combinations (actions)
  - `do_idle:            push == 0 && pop == 0`
  - `do_pop:             push == 0 && pop == 1`
  - `do_push:            push == 1 && pop == 0`
  - `do_push_pop:        push == 1 && pop == 1`



# FIFO Controller

## Status Flags

---

- Two status flags to affect the state transition (why?)
  - ◆ `fifo_almost_empty`: `tail == head - 1`
  - ◆ `fifo_almost_full`: `head == tail - 1`
- Some flags determined by states
  - ◆ `fifo_empty` = 1 at EMPTY state
  - ◆ `fifo_full` = 1 at FULL state
  - ◆ `oen` = 0 at READOUT state
    - ▣ Or you can keep it low constantly

# FIFO Controller

## Error Flags

---

- `fifo_error = 1`
  - ◆ Whenever both push and pop are activated at the same time
  - ◆ When pop is activated at EMPTY state
  - ◆ When push is activated at FULL state
  - ◆ When push or pop is activated at READOUT state

# FIFO Controller


## Execution

---

- Pushing (write) takes one clock cycle
- Popping (read) takes two clock cycles (why?)
- The state diagram is the spec
  - ◆ Is the state diagram (in the next slide) complete?
  - ◆ When in doubt, verify the state diagram and modify the RTL code accordingly

# State Diagram

What is head\_plus?

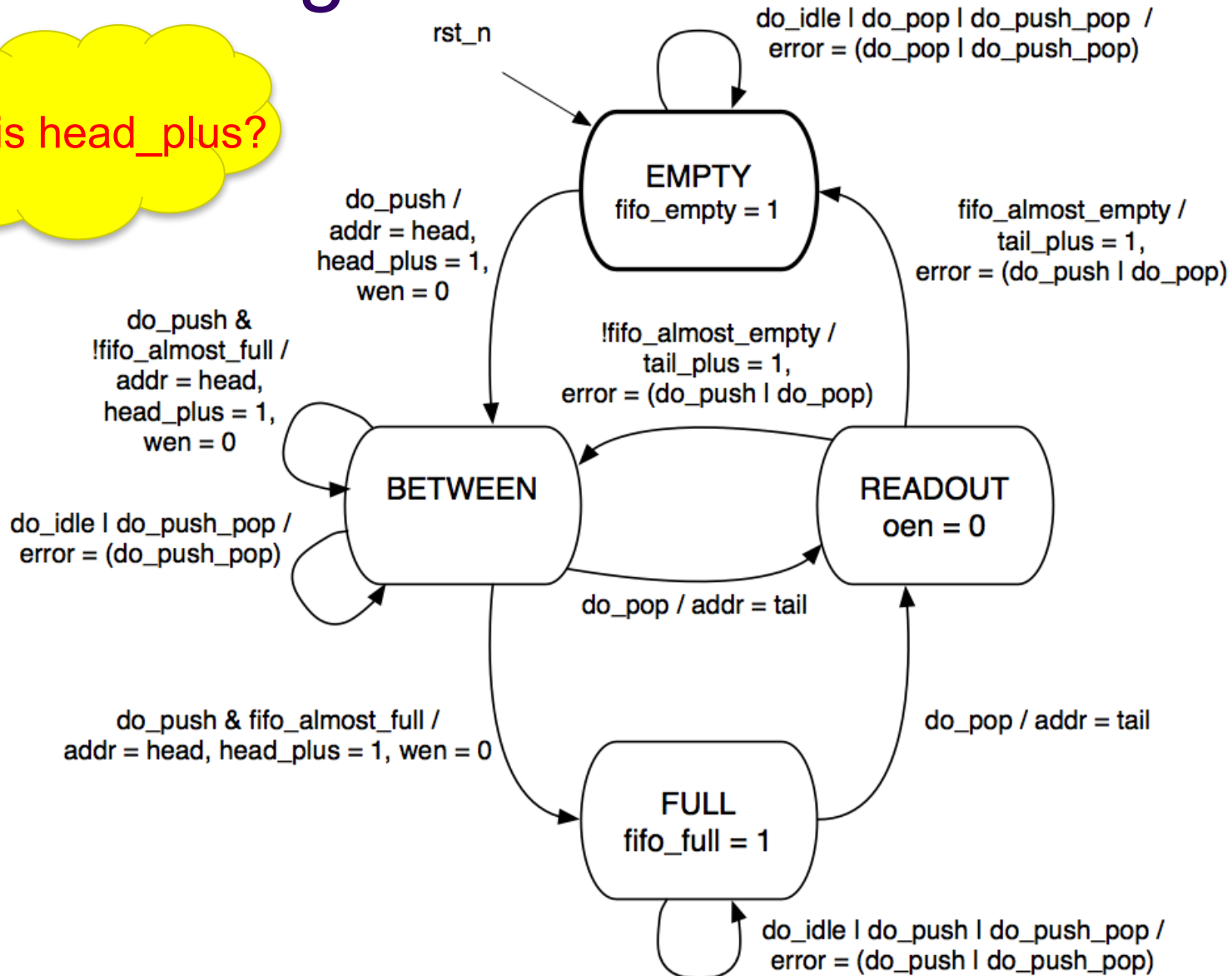

# Note and Hint:

## Generating Flags with Head/Tail Pointers

- **Potentially Buggy Verilog code**

(tail = 4'b1111, head = 4'b0000)

```
always @(tail or head) begin
    if (tail == head - 1) begin
        fifo_almost_empty = 1;
    end else begin
        fifo_almost_empty = 0;
    end
end

.....

end
```

always @\* begin

tail == head - 1'b1

# Note and Hint:

## Try to symbolize every condition

---

```
always @(head_plus or head) begin
    if (head_plus == 1'b1) begin
        head_next = head + 1'b1;
    end else begin
        head_next = head;
    end
end
```

# Guideline of Verilog Design (1/2)

---

- Prepare the block diagram and FSM well
  - ◆ Before your Verilog coding
- FSM: the simpler the better
  - ◆ Try to symbolize every condition for state transition
  - ◆ One single state can take multiple cycles
  - ◆ States can be nested

# Guideline of Verilog Design (2/2)

---

- There is no best style for every design
  - ◆ State arrangement
  - ◆ Naming convention
    - ▣ With `fifo_` or without `fifo_` (`do_`)
- This FIFO design can be improved
  - ◆ E.g., with pipelined architecture, etc.
- The order of `always` (or `assign`) blocks does not matter



# Memory Block: Description

---


- Single-port synchronous SRAM
- Behavior model: `RAM32x8.v`
  - ◆ Simulation only
  - ◆ Non-synthesizable
  - ◆ Black box

# Memory Block: IO Interface

---

## Pin Description

Pin	Description
A[4:0]	Addresses (A[0] = LSB)
D[7:0]	Data Inputs (D[0] = LSB)
CLK	Clock Input
CEN	Chip Enable
WEN	Write Enable
OEN	Output Enable
Q[7:0]	Data Outputs (Q[0] = LSB)

 

# Assignment

---

- Complete your own FIFO module
- There is a design template
  - ◆ `hw03_fifo2017.tgz`
- How to extract the tar-gzipped file
  - `$ tar zxvf hw03_fifo2017.tgz`
- Refer to `00_README.txt` carefully
  - ◆ File list with short description
  - ◆ How to avoid timing violation in RTL simulation?
  - ◆ How to synthesis with SRAM block?

# FIFO Design Part 1

---

- Complete the 32x8 FIFO design with the given memory model
- You should improve the stimulus and verify the design as complete as you can
- Use nWave's debug features, e.g., alias table to help the signal debugging of state vector and control signals
- Try to use as many as previous simulation techniques we mentioned

# FIFO Design Part 2

---

- Extend the FIFO to 64x16
  - ◆ Using the 32x8 memory as a basic block
  - ◆ You cannot modify RAM32x8.v
  - ◆ Instead, you may use multiple (hint: four) 32x8 memory blocks
- Prepare proper test patterns to validate your design
- Perform the synthesis

# Write a Summary Report

---

- Show that you can or can not access
  - ◆ Every state
  - ◆ Every state transition
  - ◆ Every condition to trigger a transition
- Improve your testbench and try to maximize the accessibility
- Discussion: can you improve the latency of popping (e.g., with the pipeline of consecutive reads)?
- Discussion: how can you modify the FIFO to a Stack (i.e., first-in last-out)?

# A Few More Note for You

---

- Many of you ask for a "good" RTL coding sample.
  - ◆ Well, this is a good design example instead, with an explicit finite state machine and its datapath.
- So please treat it not only a simple homework assignment but also a design pattern.
  - ◆ Take a careful study in the design structure and style.
- Let me know if you encounter problem.
- Have fun with your designing!